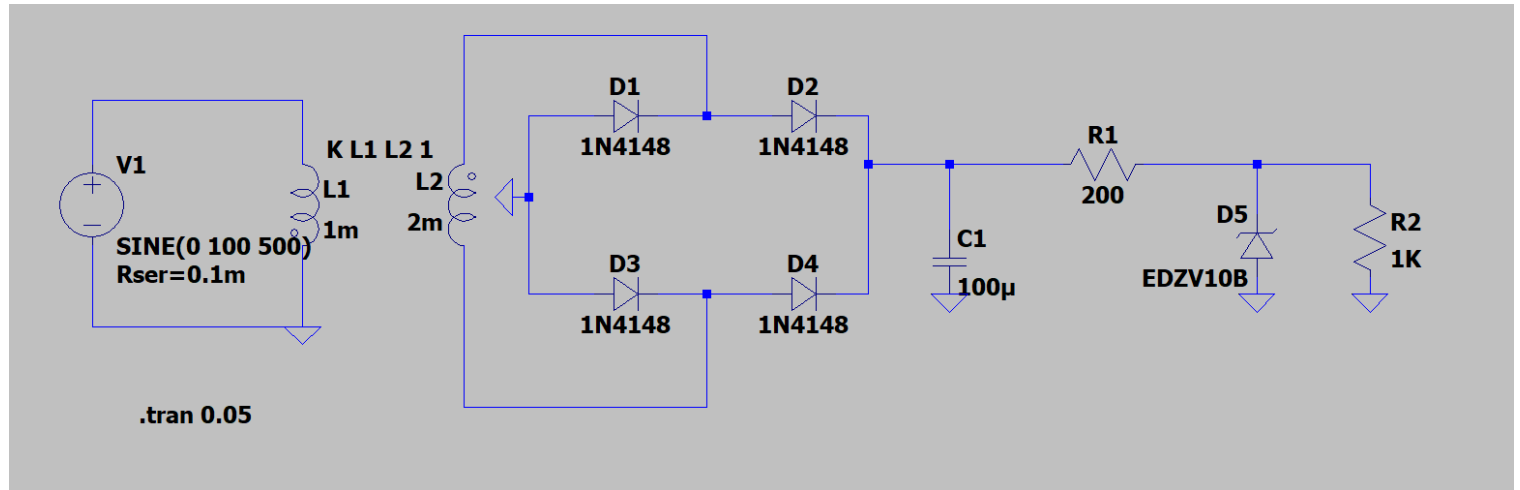


# SIMULATION OF SYSTEM-DC POWER SUPPLY



## **CIRCUIT COMPONENTS :**

- Ac voltage source
- Transformer
- 4 X 1N4148 diode
- 1 x 100μ F capacitor
- 200 Ω , 1k Ω resistors
- 1 x EDZV10B Zener diode


## **DEFINITION:**

A DC power supply circuit converts alternating current (AC) to direct current (DC) suitable for powering electronic devices and circuits.

## **NECESSITY:**

DC is foundational to modern electronics and electrical engineering. Unlike AC, where electric charge flow periodically reverses direction, DC provides a unidirectional flow of electrons.

## OVERVIEW:

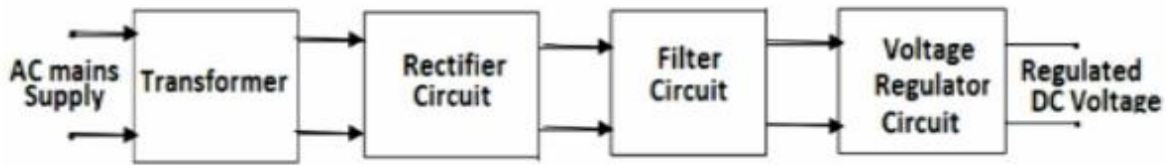


**Block Diagram of DC Regulated Power Supply**

It involves several stages that include:

1. **Transformer:** steps up or down the input AC voltage to a desired level.
2. **Rectifier:** converts AC to pulsating DC.
3. **Filter:** Smoothens the pulsating DC into a more stable DC voltage.
4. **Voltage regulator:** Maintains constant DC output voltage despite variations in input or load conditions.

## ANALOG WAVEFORMS:

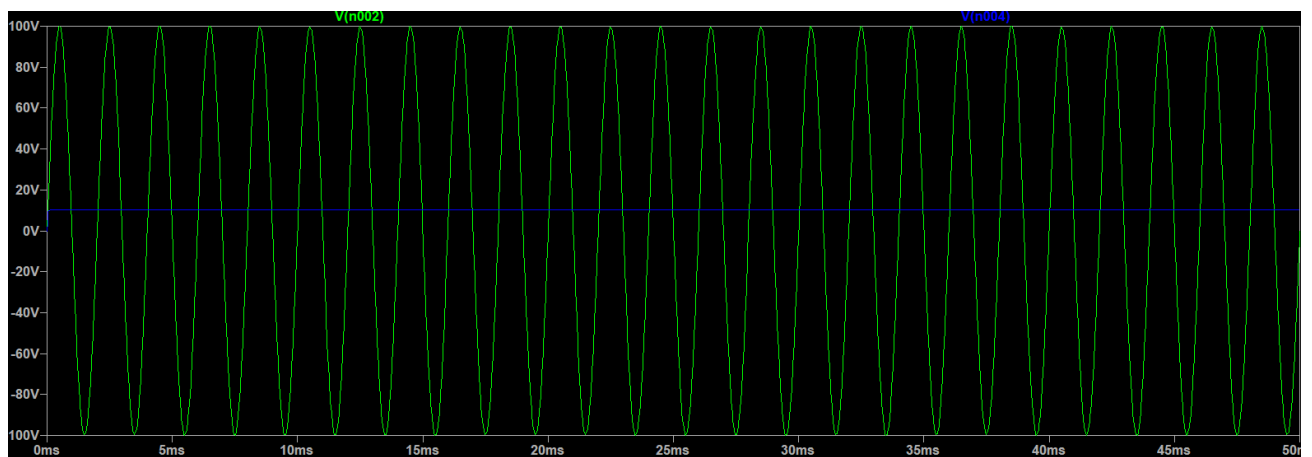

The green sine signal indicates the input signal.

The blue linear signal indicates the output signal.

## **APPLICATIONS:**

DC power supplies are widely used in various applications, including:

- Charging batteries
- Powering electronic devices (like computers and mobile phones)
- Providing power for industrial equipment